

William Horton, Andy Weekes, Tyler Martin

5/2/23

Prof. Zdravko Markov

CS 385-01

Final Report

Instruction Set Architecture:

ALU Control lines

Ainvert	Bnegate	Operation	Instruction
0	0	00	and
0	0	01	or
0	0	10	add
0	1	10	sub
0	1	11	slt
1	1	00	nor
1	1	01	nand

R Format - (ADD, SUB, AND, OR, NOR, NAND,SLT)

op	rs	rt	rd	unused
4	2	2	2	6

I Format - (ADDI, LW, SW, BEQ, BNE)

op	rs	rt	address/value
4	2	2	8

Instruction	Code	Format	Meaning
ADD	0000	R-Type	add \$t1, \$t2, \$t3 ADD = Addition \$t1 = the result of \$t2 + \$t3
SUB	0001	R-Type	sub \$t1, \$t2, \$t3 SUB = Subtraction \$t1 = the result of \$t2 - \$t3
AND	0010	R-Type	and \$t1, \$t2, \$t3 AND = Bitwise <i>AND</i> \$t1 = result of \$t2 <i>AND</i> \$t3
OR	0011	R-Type	or \$t1, \$t2, \$t3 OR = Bitwise <i>OR</i> \$t1 = the result of \$t2 <i>OR</i> \$t3
NOR	0100	R-Type	nor \$t1, \$t2, \$t3 NOR = Bitwise <i>NOR</i> \$t1 = the result of \$t2 <i>NOR</i> \$t3
NAND	0101	R-Type	nand \$t1, \$t2, \$t3 NAND = Bitwise <i>NAND</i> \$t1 = the result of \$t2 <i>NAND</i> \$t3
SLT	0110	R-Type	slt \$t1, \$t2, \$t3 SLT = Set Less Than \$t1 = 1 if \$t2 < \$t3 \$t1 = 0 if \$t2 ≥ \$t3 \$t2 - variable to be checked \$t3 - variable to be checked with
ADDI	0111	I-Type	addi \$t1, \$0, value ADDI - Add immediate value \$t1 = value \$0 - Source Register \$t1 - Destination Register value - Immediate value to be added to \$t1
BEQ	1010	I-Type	beq \$t1, \$t2, immed BEQ = Branch if Equal Program jumps "immed" if \$t1 = \$t2


Instruction	Code	Format	Meaning
BNE	1011	I-Type	bne \$t1, \$t2, immed BNE = Branch if Not Equal Program jumps "immed" as long as \$t1 does not equal \$t2
LW	1000	I-Type	lw \$t0, offset(\$t1) LW = Load Word Loads word (32 Bit) from \$t1 plus the offset in bits and stores it in \$t0
SW	1001	I-Type	sw \$t0, offset(\$t1) SW = Store Word Stores word (32 Bit) from \$t0 to \$t1 plus the offset in bits

Logic Diagrams / Truth Tables:


Truth Table for Main Control

Instruction	Input(OP)	Output(Control)							
	OP	RegDst	ALUSrc	MemtoReg	RegWrite	MemWrite	Reg. Inc	ALUSrc	
ADD	0000	1	0	0	1	0	0	0	0010
SUB	0001	1	0	0	1	0	0	0	0110
AND	0010	1	0	0	1	0	0	0	0000
OR	0011	1	0	0	1	0	0	0	0001
NOR	0100	1	0	0	1	0	0	0	1100
NAND	0101	1	0	0	1	0	0	0	0101
SLT	0110	1	0	0	1	0	0	0	0111
ADDI	0111	0	1	0	1	0	0	0	0010
LW	1000	0	1	1	1	0	0	0	0010
SW	1001	0	1	0	0	1	0	0	0010
BEQ	1010	0	0	0	0	0	1	0	0110
BNE	1011	0	0	0	0	0	0	1	0110


Final CPU

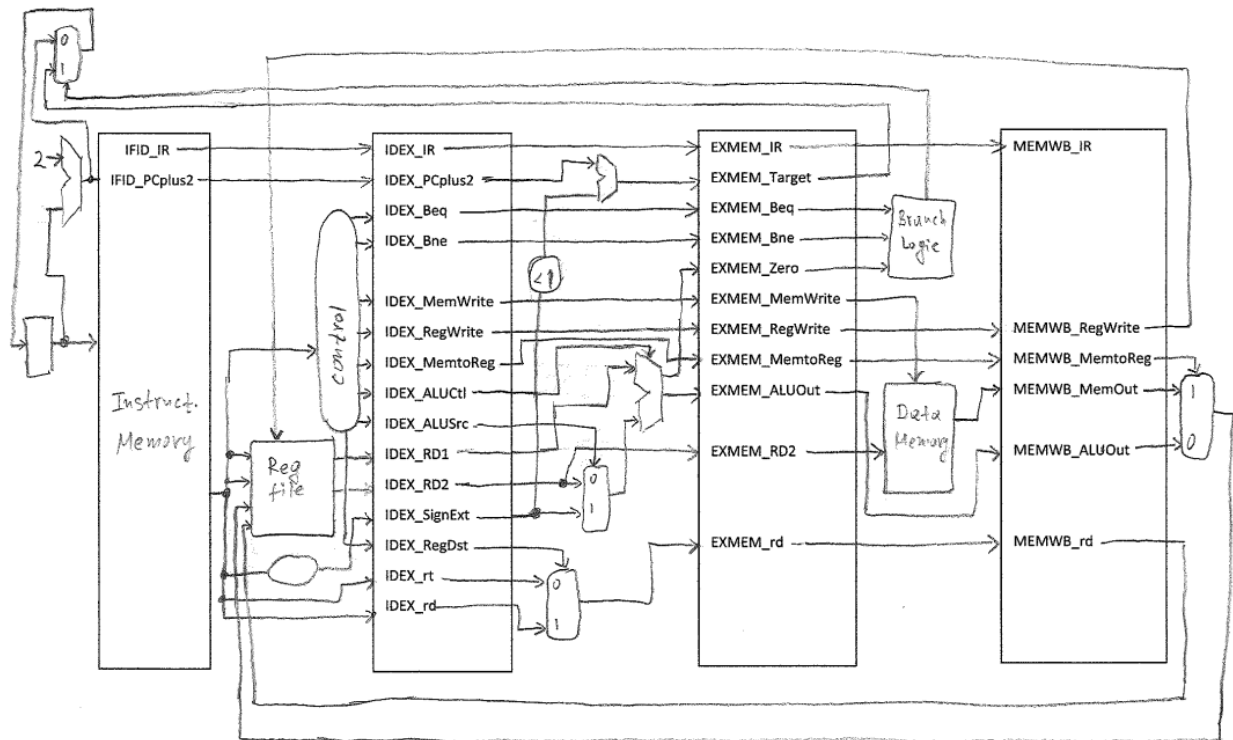


16 Bit ALU

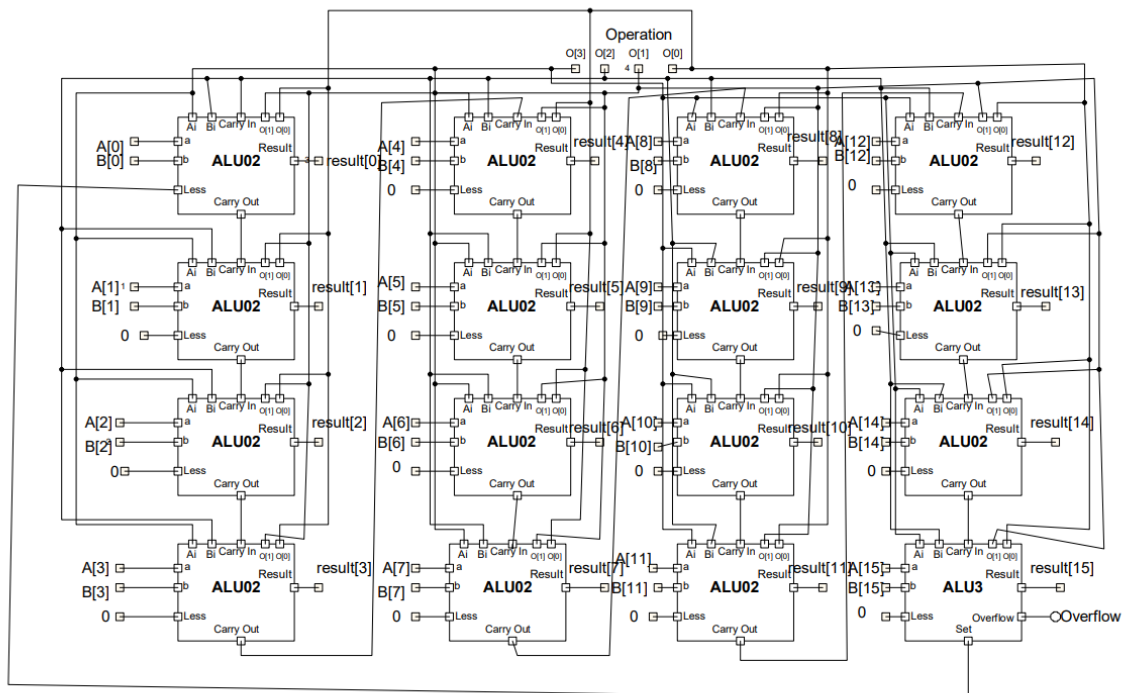


ALU 0, 1, 2, ..., 14

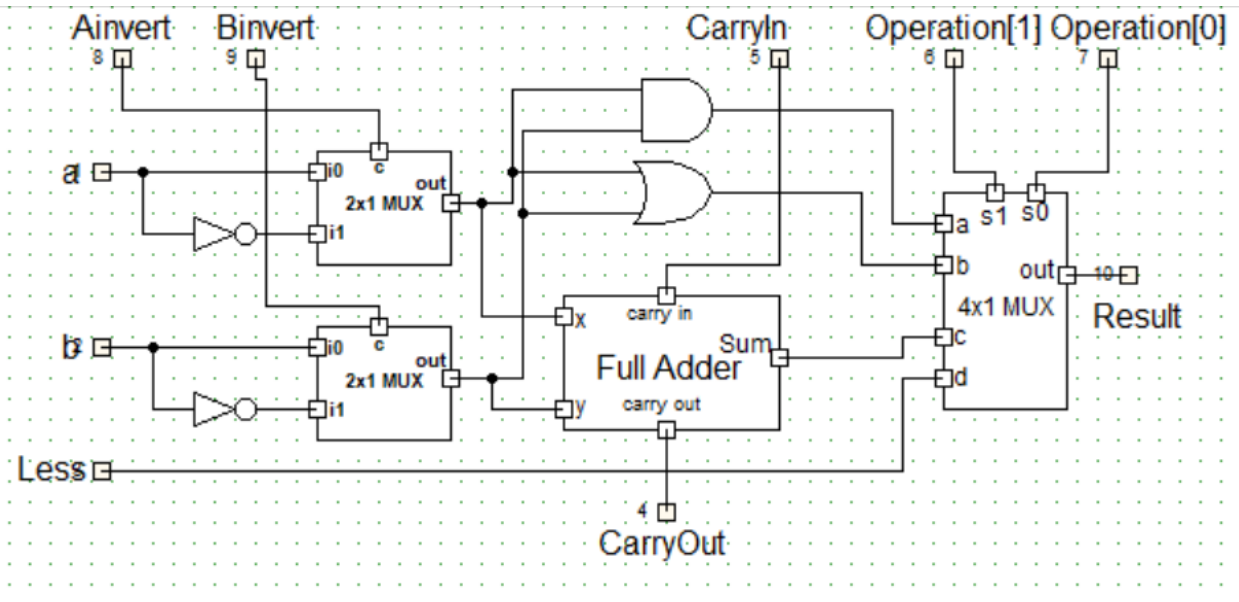


ALU 15

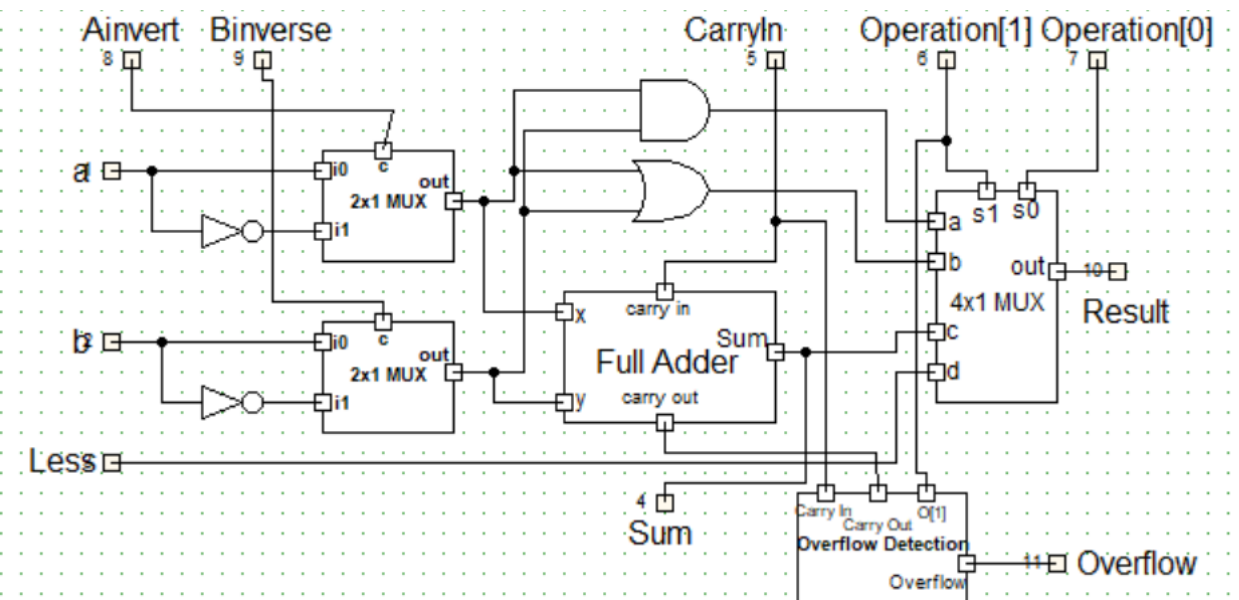


Overflow Detection

 


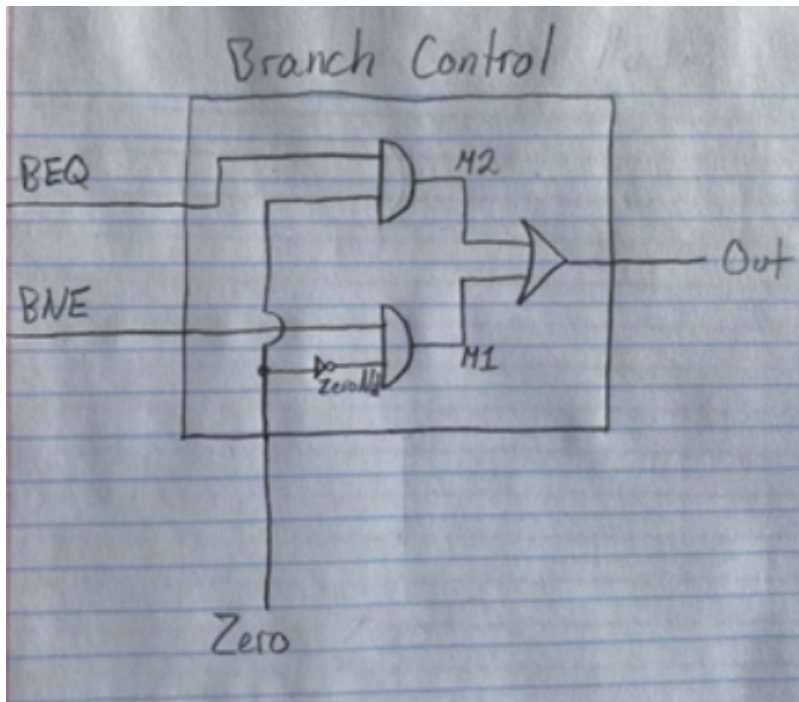


Half Adder

 


Full Adder

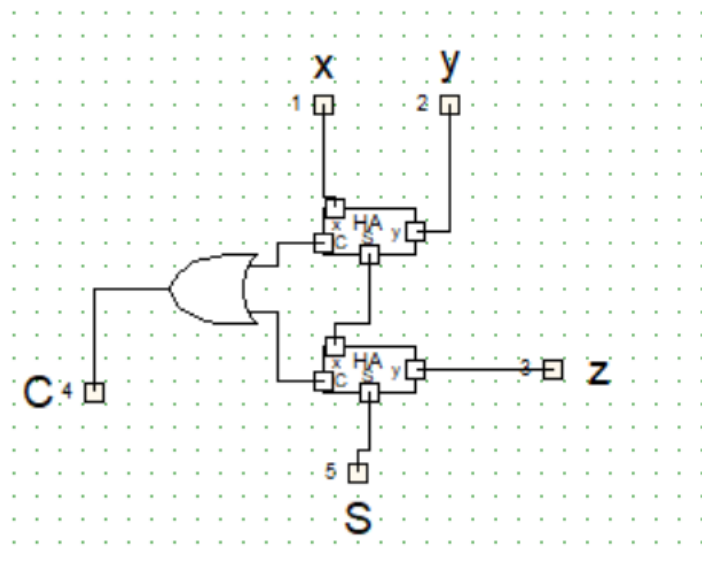


2x1 Multiplexer

 


4x1 Multiplexer

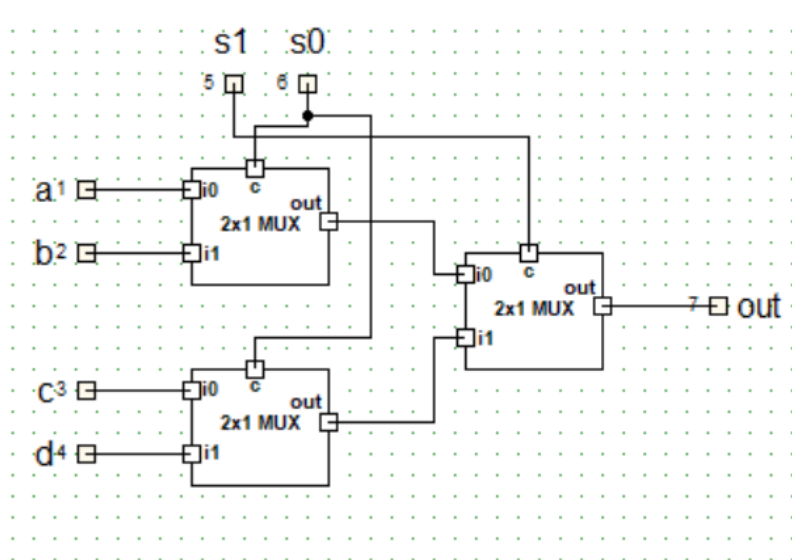

2 Bit 2x1 Multiplexer

 

16 Bit 2x1 Multiplexer

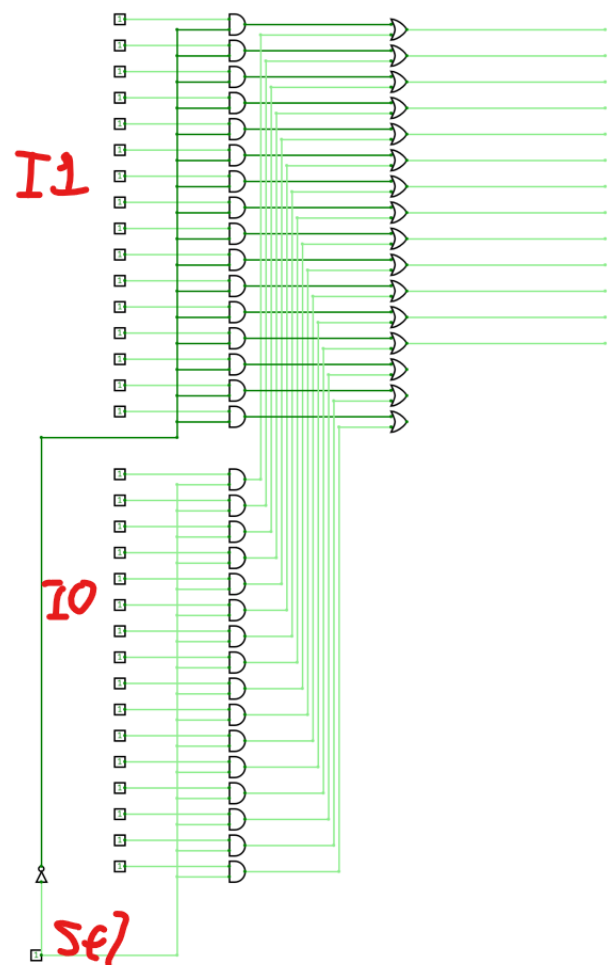

Verilog Source Code:

```
// Behavioral model of MIPS - pipelined implementation

// CS 385-01 Progress Report 4
// by Andrew Weekes, William Horton, and Tyler Martin

// register file module
module reg_file (RR1,RR2,WR,WD,RegWrite,RD1,RD2,clock);
    input [1:0] RR1,RR2,WR;
    input [15:0] WD;
    input RegWrite,clock;
    output [15:0] RD1,RD2;
    reg [15:0] Regs[0:3];
    assign RD1 = Regs[RR1];
    assign RD2 = Regs[RR2];
    initial Regs[0] = 0;
    always @(negedge clock)
        if (RegWrite==1 & WR!=0)
            Regs[WR] <= WD;
endmodule

// 16-bit MIPS ALU in Verilog (1-bit ALU behavioral implementation)
module alu (op,a,b,result,zero);

    // 16 bit A and B
    input [15:0] a;
    input [15:0] b;

    // op is same, result is 16 bits
    input [3:0] op;
    output [15:0] result;
    output zero;

    // change to 16 1 bit ALUs
    ALU1 alu0 (a[0],b[0],op[3],op[2],op[1:0],set, op[2],c1,result[0]);
    ALU1 alu1 (a[1],b[1],op[3],op[2],op[1:0],1'b0,c1, c2,result[1]);
    ALU1 alu2 (a[2],b[2],op[3],op[2],op[1:0],1'b0,c2, c3,result[2]);

    ALU1 alu3 (a[3],b[3],op[3],op[2],op[1:0],1'b0,c3, c4,result[3]);
    ALU1 alu4 (a[4],b[4],op[3],op[2],op[1:0],1'b0,c4, c5,result[4]);
    ALU1 alu5 (a[5],b[5],op[3],op[2],op[1:0],1'b0,c5, c6,result[5]);
    ALU1 alu6 (a[6],b[6],op[3],op[2],op[1:0],1'b0,c6, c7,result[6]);
    ALU1 alu7 (a[7],b[7],op[3],op[2],op[1:0],1'b0,c7, c8,result[7]);
    ALU1 alu8 (a[8],b[8],op[3],op[2],op[1:0],1'b0,c8, c9,result[8]);
    ALU1 alu9 (a[9],b[9],op[3],op[2],op[1:0],1'b0,c9, c10,result[9]);
    ALU1 alu10(a[10],b[10],op[3],op[2],op[1:0],1'b0,c10, c11,result[10]);
    ALU1 alu11(a[11],b[11],op[3],op[2],op[1:0],1'b0,c11, c12,result[11]);
    ALU1 alu12(a[12],b[12],op[3],op[2],op[1:0],1'b0,c12, c13,result[12]);
    ALU1 alu13(a[13],b[13],op[3],op[2],op[1:0],1'b0,c13, c14,result[13]);
    ALU1 alu14(a[14],b[14],op[3],op[2],op[1:0],1'b0,c14, c15,result[14]);

    ALUmsb alu15 (a[15],b[15],op[3],op[2],op[1:0],1'b0,c15, c16,result[15],set);
    nor nor1(zero,
result[0],result[1],result[2],result[3],result[4],result[5],result[6],result[7],result[8],result[9],result[10],result[11],result[12],result[13],result[14],result[15]);
endmodule

// 1-bit ALU for bits 0-2
module ALU1 (a,b,ainvert,binvert,op,less,carryin,carryout,result);
    input a,b,less,carryin,ainvert,binvert;
```



```

input [1:0] op;
output carryout, result;

// beginning gate level
//create inverses
not (aNot,a);
not (bNot,b);

// if both binvert and !Ainverse, then either NOR or NAND

// 2x1 multiplexer and Ainverse and Binverse
multi2x1 a1(a,aNot,ainvert,aOut);
multi2x1 b1(b,bNot,binvert,bOut);

// AND or NOR operation
and (andOut,aOut,bOut);

// OR or NAND operation
or (orOut,aOut,bOut);

// SUM or SUB operation
fulladder fa(sum,carryout,aOut,bOut,carryin);

// 4x1 multiplexer
multi4x1 r1(andOut,orOut,sum,less,op[1],op[0],result);
endmodule

// 1-bit ALU for the most significant bit
module ALUmsb (a,b,ainvert,binvert,op,less,carryin,carryout,result,sum);
input a,b,less,carryin,ainvert,binvert;
input [1:0] op;
output carryout,sum, result;

// beginning gate level
//create inverses
not (aNot,a);
not (bNot,b);

// if both binvert and !Ainverse, then either NOR or NAND

// 2x1 multiplexer and Ainverse and Binverse
multi2x1 a1(a,aNot,ainvert,aOut);
multi2x1 b1(b,bNot,binvert,bOut);

// AND or NOR operation
and (andOut,aOut,bOut);

// OR or NAND operation
or (orOut,aOut,bOut);

// SUM or SUB operation
fulladder fa(sum,carryout,aOut,bOut,carryin);

// 4x1 multiplexer
multi4x1 r1(andOut,orOut,sum,less,op[1],op[0],result);

// Overflow detection, not using xor as possibility of negated B when doing subtraction not causing overflow

xor(overflow1,carryin,carryout);
and(Overflow,overflow1,op[1]);

```

```
endmodule
```

```
// Support Modules
```

```
// Description of half adder (see Fig 4-5b)
```

```
module halfadder (S,C,x,y);
```

```
    input x,y;
```

```
    output S,C;
```

```
//Instantiate primitive gates
```

```
    xor (S,x,y);
```

```
    and (C,x,y);
```

```
endmodule
```

```
//Description of full adder (see Fig 4-8)
```

```
module fulladder (S,C,x,y,z);
```

```
    input x,y,z;
```

```
    output S,C;
```

```
    wire S1,D1,D2; //Outputs of first XOR and two AND gates
```

```
//Instantiate the halfadder
```

```
    halfadder HA1 (S1,D1,x,y),
```

```
                HA2 (S,D2,S1,z);
```

```
    or g1(C,D2,D1);
```

```
endmodule
```

```
// 2x1 multiplexer
```

```
module multi2x1(x,y,z,out);
```

```
    input x,y,z;
```

```
    output out;
```

```
// possibly other order?
```

```
    not n1(zn,z);
```

```
    and a1(m1,y,z),
```

```
        a2(m2,x,zn);
```

```
    or o1(out,m1,m2);
```

```
endmodule
```

```
// 4x1 multiplexer
```

```
module multi4x1(a,b,c,d,s1,s0,out);
```

```
    input a,b,c,d,s1,s0;
```

```
    output out;
```

```
    multi2x1 m1(a,b,s0,c0);
```

```
    multi2x1 m2(c,d,s0,c1);
```

```
    multi2x1 m3(c0,c1,s1,out);
```

```
endmodule
```

```
module branchControlMux(Bne, Beq, Zero, Out);
```

```
    input Beq, Bne, Zero;
```

```
    output Out;
```

```
    not n1(ZeroNot, Zero);
```

```
    and a1(m1, Bne, ZeroNot),
```

```
        a2(m2, Beq, Zero);
```

```
    or o1(Out, m1, m2);
```

```
endmodule
```

```
module MainControl (Op,Control);
```

```
    input [3:0] Op;
```

```
    output reg [10:0] Control;
```

```
// RegDst,ALUSrc,MemtoReg,RegWrite,MemWrite,Beq,Bne, = 1 bit; ALUctl = 4 bits; Total = 11 bits
```

```
always @(Op) case (Op)
```

```

//R-type instructions
4'b0000: Control <= 11'b10010_00_0010; // Rtype - ADD - complete
4'b0001: Control <= 11'b10010_00_0110; // Rtype - SUB - complete
4'b0010: Control <= 11'b10010_00_0000; // Rtype - AND - complete
4'b0011: Control <= 11'b10010_00_0001; // Rtype - OR - complete
4'b0100: Control <= 11'b10010_00_1100; // Rtype - NOR - complete
4'b0101: Control <= 11'b10010_00_1101; // Rtype - NAND - complete
4'b0110: Control <= 11'b10010_00_0111; // Rtype - SLT - complete

//I-type instructions
4'b0111: Control <= 11'b01010_00_0010; // Itype - ADDI - complete
4'b1000: Control <= 11'b01110_00_0010; // LW - last 4 bits = code for add because LW adds offset to base register - complete
4'b1001: Control <= 11'b01001_00_0010; // SW -
4'b1010: Control <= 11'b00000_10_0110; // BEQ - last 4 bits = code for sub because BEQ subtracts address - complete
4'b1011: Control <= 11'b00000_01_0110; // BNE - last 4 bits = code for sub because BNE subtracts address - complete
endcase
endmodule

// Gate Level 2 bit 2x1 Multiplexer - if Sel is true - return first term, if false - return second term
module double2x1mux (I0,I1,Sel,Out);
input [1:0] I0,I1;
input Sel;
output wire [1:0] Out;

// gate level - done
not (Selnot,Sel);

// A and gates
and (Aand1,I1[1],Selnot);
and (Aand0,I1[0],Selnot);

// B and gates

and (Band1,I0[1],Sel);
and (Band0,I0[0],Sel);

// Final Or Gates for Output

or (Out[1],Aand1,Band1);
or (Out[0],Aand0,Band0);

endmodule

// Gate Level Quad 2x1 Multiplexer - if Sel is true - return first term, if false - return second term
module hexabit2x1mux (I0,I1,Sel,Out);
input [15:0] I0,I1;
input Sel;
output wire [15:0] Out;

// gate level - done
not (Selnot,Sel);

// A and gates
and (Aand15,I1[15],Selnot);
and (Aand14,I1[14],Selnot);
and (Aand13,I1[13],Selnot);
and (Aand12,I1[12],Selnot);
and (Aand11,I1[11],Selnot);
and (Aand10,I1[10],Selnot);
and (Aand9,I1[9],Selnot);
and (Aand8,I1[8],Selnot);

```

```

and (Aand7,I1[7],Selnot);
and (Aand6,I1[6],Selnot);
and (Aand5,I1[5],Selnot);
and (Aand4,I1[4],Selnot);
and (Aand3,I1[3],Selnot);
and (Aand2,I1[2],Selnot);
and (Aand1,I1[1],Selnot);
and (Aand0,I1[0],Selnot);

```

```

// B and gates
and (Band15,I0[15],Sel);
and (Band14,I0[14],Sel);
and (Band13,I0[13],Sel);
and (Band12,I0[12],Sel);
and (Band11,I0[11],Sel);
and (Band10,I0[10],Sel);
and (Band9,I0[9],Sel);
and (Band8,I0[8],Sel);
and (Band7,I0[7],Sel);
and (Band6,I0[6],Sel);
and (Band5,I0[5],Sel);
and (Band4,I0[4],Sel);
and (Band3,I0[3],Sel);
and (Band2,I0[2],Sel);
and (Band1,I0[1],Sel);
and (Band0,I0[0],Sel);

```

```

// Final Or Gates for Output
or (Out[15],Aand15,Band15);
or (Out[14],Aand14,Band14);
or (Out[13],Aand13,Band13);
or (Out[12],Aand12,Band12);
or (Out[11],Aand11,Band11);
or (Out[10],Aand10,Band10);
or (Out[9],Aand9,Band9);
or (Out[8],Aand8,Band8);
or (Out[7],Aand7,Band7);
or (Out[6],Aand6,Band6);
or (Out[5],Aand5,Band5);
or (Out[4],Aand4,Band4);
or (Out[3],Aand3,Band3);
or (Out[2],Aand2,Band2);
or (Out[1],Aand1,Band1);
or (Out[0],Aand0,Band0);

```

```

endmodule

```

```

// PART OF OLD MIPS - DONT NEED IT - EVERYTHING COMES FROM MAIN CONTROL

```

```

module CPU (clock,PC,IFID_IR,IDEX_IR,EXMEM_IR,MEMWB_IR,WD);
input clock;
output [15:0] PC,IFID_IR,IDEX_IR,EXMEM_IR,MEMWB_IR,WD;

```

```

initial begin

```

```

// Program: swap memory cells (if needed) and compute absolute value |5-7|=2

```

```

// ----Program with nop's----

```

```

IMemory[0] = 16'b1000_00_01_00000000; // lw $1, 0($0)
IMemory[1] = 16'b1000_00_10_00000010; // lw $2, 2($0)
IMemory[2] = 16'b0000000000000000; // nop
IMemory[3] = 16'b0000000000000000; // nop

```

```

IMemory[4] = 16'b0000000000000000; // nop
IMemory[5] = 16'b0110_01_10_11_000000; // slt $3, $1, $2
IMemory[6] = 16'b0000000000000000; // nop
IMemory[7] = 16'b0000000000000000; // nop
IMemory[8] = 16'b0000000000000000; // nop
IMemory[9] = 16'b1010_00_11_00000101; // beq $3, $0, IMemory[15]
//IMemory[9] = 16'b1011_00_11_00000101; // bne $3, $0, IMemory[15]
IMemory[10] = 16'b0000000000000000; // nop
IMemory[11] = 16'b0000000000000000; // nop
IMemory[12] = 16'b0000000000000000; // nop
IMemory[13] = 16'b1001_00_01_00000010; // sw $1, 2($0)
IMemory[14] = 16'b1001_00_10_00000000; // sw $2, 0($0)
IMemory[15] = 16'b0000000000000000; // nop
IMemory[16] = 16'b0000000000000000; // nop
IMemory[17] = 16'b0000000000000000; // nop
IMemory[18] = 16'b1000_00_01_00000000; // lw $1, 0($0)
IMemory[19] = 16'b1000_00_10_00000010; // lw $2, 2($0)
IMemory[20] = 16'b0000000000000000; // nop
IMemory[21] = 16'b0000000000000000; // nop
IMemory[22] = 16'b0000000000000000; // nop
IMemory[23] = 16'b0100_10_10_10_000000; // nor $2, $2, $2 (sub $3, $1, $2 in two's complement)
IMemory[24] = 16'b0000000000000000; // nop
IMemory[25] = 16'b0000000000000000; // nop
IMemory[26] = 16'b0000000000000000; // nop
IMemory[27] = 16'b0111_10_10_00000001; // addi $2, $2, 1
IMemory[28] = 16'b0000000000000000; // nop
IMemory[29] = 16'b0000000000000000; // nop
IMemory[30] = 16'b0000000000000000; // nop
IMemory[31] = 16'b0000_01_10_11_000000; // add $3, $1, $2

// ----Program without nop's
// IMemory[0] = 16'b1000_00_01_00000000; // lw $1, 0($0)
// IMemory[1] = 16'b1000_00_10_00000010; // lw $2, 2($0)
// IMemory[2] = 16'b0110_01_10_11_000000; // slt $3, $1, $2
// IMemory[3] = 16'b1010_00_11_00000101; // beq $3, $0, IMemory[15]
// //IMemory[3] = 16'b1011_00_11_00000101; // bne $3, $0, IMemory[15]
// IMemory[4] = 16'b1001_00_01_00000010; // sw $1, 2($0)
// IMemory[5] = 16'b1001_00_10_00000000; // sw $2, 0($0)
// IMemory[6] = 16'b1000_00_01_00000000; // lw $1, 0($0)
// IMemory[7] = 16'b1000_00_10_00000010; // lw $2, 2($0)
// IMemory[8] = 16'b0100_10_10_10_000000; // nor $2, $2, $2 (sub $3, $1, $2 in two's complement)
// IMemory[9] = 16'b0111_10_10_00000001; // addi $2, $2, 1
// IMemory[10] = 16'b0000_01_10_11_000000; // add $3, $1, $2

// Data
DMemory[0] = 16'd5; // switch the cells and see how the simulation output changes
DMemory[1] = 16'd7; // (beq is taken if DMemory[0]=7; DMemory[1]=5, not taken otherwise)
end

// VERY SIMILAR TO LAST PROJECT - ALL EXPLAINED ON DIAGRAM
// Pipeline
// IF
wire [15:0] PCplus2, NextPC;
reg[15:0] PC, IMemory[0:1023], IFID_IR, IFID_PCplus2;
alu_fetch (4'b0010, PC, 16'd2, PCplus2, Unused1);
// SHOULD BE BRANCHING LOGIC WHERE BRANCH IS
//assign NextPC = (EXMEM_Beq && EXMEM_Zero || EXMEM_Bne && ~EXMEM_Zero) ? EXMEM_Target: PCplus2;
//hexabit2x1mux BranchControl(EXMEM_Target, PCplus2, (EXMEM_Beq && EXMEM_Zero || EXMEM_Bne &&
~EXMEM_Zero), NextPC);
hexabit2x1mux BranchControl2(EXMEM_Target, PCplus2, BranchOutput, NextPC);

```

```

// ID
wire [10:0] Control;
reg IDEX_RegWrite, IDEX_MemtoReg,
    IDEX_Beq, IDEX_Bne, IDEX_MemWrite,
    IDEX_ALUSrc, IDEX_RegDst;
reg [3:0] IDEX_ALUctl; // MUST BE ALU CTL - 4 bits
wire [15:0] RD1, RD2, SignExtend, WD;
reg [15:0] IDEX_PCplus2, IDEX_RD1, IDEX_RD2, IDEX_SignExt, IDEXE_IR;
reg [15:0] IDEX_IR; // For monitoring the pipeline
reg [1:0] IDEX_rt, IDEX_rd;
reg MEMWB_RegWrite; // part of MEM stage, but declared here before use (to avoid error)
reg [1:0] MEMWB_rd; // part of MEM stage, but declared here before use (to avoid error)
reg _file rf (IFID_IR[11:10], IFID_IR[9:8], MEMWB_rd, WD, MEMWB_RegWrite, RD1, RD2, clock);
MainControl MainCtr (IFID_IR[15:12], Control);
assign SignExtend = {{8{IFID_IR[7]}} , IFID_IR[7:0]};

// EXE
reg EXMEM_RegWrite, EXMEM_MemtoReg,
    EXMEM_Beq, EXMEM_Bne, EXMEM_MemWrite;
wire [15:0] Target;
reg EXMEM_Zero;
reg [15:0] EXMEM_Target, EXMEM_ALUOut, EXMEM_RD2;
reg [15:0] EXMEM_IR; // For monitoring the pipeline
reg [1:0] EXMEM_rd;
wire [15:0] B, ALUOut;
wire [3:0] ALUctl;
wire [1:0] WR;
alu branch (4'b0010, IDEX_SignExt<<1, IDEX_PCplus2, Target, Unused2);
// set out of order

alu ex (IDEX_ALUctl, IDEX_RD1, B, ALUOut, Zero);
// REMOVE - set ALUctl to complete control code
assign B = (IDEX_ALUSrc) ? IDEX_SignExt: IDEX_RD2; // ALUSrc Mux
assign WR = (IDEX_RegDst) ? IDEX_rd: IDEX_rt; // RegDst Mux

// MEM
reg MEMWB_MemtoReg;
reg [15:0] DMemory[0:1023], MEMWB_MemOut, MEMWB_ALUOut;
reg [15:0] MEMWB_IR; // For monitoring the pipeline
wire [15:0] MemOut;
assign MemOut = DMemory[EXMEM_ALUOut>>1];
branchControlMux BranchControl1(EXMEM_Bne, EXMEM_Beq, EXMEM_Zero, BranchOutput);
always @(negedge clock) if (EXMEM_MemWrite) DMemory[EXMEM_ALUOut>>1] <= EXMEM_RD2;

// WB
assign WD = (MEMWB_MemtoReg) ? MEMWB_MemOut: MEMWB_ALUOut; // MemtoReg Mux

initial begin
    PC = 0;
// Initialize pipeline registers

IDEX_RegWrite=1'b0;IDEX_MemtoReg=1'b0;IDEX_Beq=1'b0;IDEX_Bne=1'b0;IDEX_MemWrite=1'b0;IDEX_ALUSrc=1'b0;IDEX_RegDst=
1'b0;
    IFID_IR=1'b0;
    EXMEM_RegWrite=1'b0;EXMEM_MemtoReg=1'b0;EXMEM_Beq=1'b0;EXMEM_Bne=1'b0;EXMEM_MemWrite=1'b0;
    EXMEM_Target=1'b0;
    MEMWB_RegWrite=1'b0;MEMWB_MemtoReg=1'b0;
end

// Running the pipeline
always @(negedge clock) begin
// IF
    PC <= NextPC;

```

```

IFID_PCplus2 <= PCplus2;
IFID_IR <= IMemory[PC>>1];
// ID
IDEX_IR <= IFID_IR; // For monitoring the pipeline
// MUST BE BOTH IDEX_BNE AND BEQ
{IDEX_RegDst, IDEX_ALUSrc, IDEX_MemtoReg, IDEX_RegWrite, IDEX_MemWrite, IDEX_Beq, IDEX_Bne, IDEX_ALUctl} <= Control;
IDEX_PCplus2 <= IFID_PCplus2;
IDEX_RD1 <= RD1;
IDEX_RD2 <= RD2;
IDEX_SignExt <= SignExtend;
IDEX_rt <= IFID_IR[9:8];
IDEX_rd <= IFID_IR[7:6];
// EXE
EXMEM_IR <= IDEX_IR; // For monitoring the pipeline
EXMEM_RegWrite <= IDEX_RegWrite;
EXMEM_MemtoReg <= IDEX_MemtoReg;
// BOTH BNE AND BEQ
EXMEM_Beq <= IDEX_Beq;
EXMEM_Bne <= IDEX_Bne;

EXMEM_MemWrite <= IDEX_MemWrite;
EXMEM_Target <= Target;
EXMEM_Zero <= Zero;
EXMEM_ALUOut <= ALUOut;
EXMEM_RD2 <= IDEX_RD2;
EXMEM_rd <= WR;

// MEM
MEMWB_IR <= EXMEM_IR; // For monitoring the pipeline
MEMWB_RegWrite <= EXMEM_RegWrite;
MEMWB_MemtoReg <= EXMEM_MemtoReg;
MEMWB_MemOut <= MemOut;
MEMWB_ALUOut <= EXMEM_ALUOut;
MEMWB_rd <= EXMEM_rd;
// WB
// Register write happens on neg edge of the clock (if MEMWB_RegWrite is asserted)
end
endmodule

// Test module

module test ();
reg clock;
wire signed [15:0] PC, IFID_IR, IDEX_IR, EXMEM_IR, MEMWB_IR, WD;
CPU test_cpu(clock, PC, IFID_IR, IDEX_IR, EXMEM_IR, MEMWB_IR, WD);
always #1 clock = ~clock;
initial begin
    $display("PC IFID_IR IDEX_IR EXMEM_IR MEMWB_IR WD");
    $monitor("%3d %h %h %h %h %2d", PC, IFID_IR, IDEX_IR, EXMEM_IR, MEMWB_IR, WD);
    clock = 1;
    #69 $finish;
end
endmodule

// 4 STAGES 4 PIPELINE REGISTERS - SHOWS HOW THE INSTRUCTION TRAVELS THROUGH THE PIPELINE
// EXECUTES IN LAST STAGE

```


Test Results:

BEQ Test 1

PC	IFID_IR	IDEX_IR	EXMEM_IR	MEMWB_IR	WD
0	0000	xxxx	xxxx	xxxx	x
2	8100	0000	xxxx	xxxx	x
4	8202	8100	0000	xxxx	x
6	0000	8202	8100	0000	0
8	0000	0000	8202	8100	5
10	0000	0000	0000	8202	7
12	66c0	0000	0000	0000	0
14	0000	66c0	0000	0000	0
16	0000	0000	66c0	0000	0
18	0000	0000	0000	66c0	1
20	a305	0000	0000	0000	0
22	0000	a305	0000	0000	0
24	0000	0000	a305	0000	0
26	0000	0000	0000	a305	-1
28	9102	0000	0000	0000	0
30	9200	9102	0000	0000	0
32	0000	9200	9102	0000	0
34	0000	0000	9200	9102	2
36	0000	0000	0000	9200	0
38	8100	0000	0000	0000	0
40	8202	8100	0000	0000	0
42	0000	8202	8100	0000	0
44	0000	0000	8202	8100	7
46	0000	0000	0000	8202	5
48	4a80	0000	0000	0000	0
50	0000	4a80	0000	0000	0
52	0000	0000	4a80	0000	0
54	0000	0000	0000	4a80	-6
56	7a01	0000	0000	0000	0
58	0000	7a01	0000	0000	0
60	0000	0000	7a01	0000	0
62	0000	0000	0000	7a01	-5
64	06c0	0000	0000	0000	0
66	xxxx	06c0	0000	0000	0
68	xxxx	xxxx	06c0	0000	0
70	xxxx	xxxx	xxxx	06c0	2

BEQ Test 2

PC	IFID_IR	IDEX_IR	EXMEM_IR	MEMWB_IR	WD
0	0000	xxxx	xxxx	xxxx	x
2	8100	0000	xxxx	xxxx	x
4	8202	8100	0000	xxxx	x
6	0000	8202	8100	0000	0
8	0000	0000	8202	8100	7
10	0000	0000	0000	8202	5
12	66c0	0000	0000	0000	0
14	0000	66c0	0000	0000	0
16	0000	0000	66c0	0000	0
18	0000	0000	0000	66c0	0
20	a305	0000	0000	0000	0
22	0000	a305	0000	0000	0
24	0000	0000	a305	0000	0
30	0000	0000	0000	a305	0
32	0000	0000	0000	0000	0
34	0000	0000	0000	0000	0
36	0000	0000	0000	0000	0
38	8100	0000	0000	0000	0
40	8202	8100	0000	0000	0
42	0000	8202	8100	0000	0
44	0000	0000	8202	8100	7
46	0000	0000	0000	8202	5
48	4a80	0000	0000	0000	0
50	0000	4a80	0000	0000	0
52	0000	0000	4a80	0000	0
54	0000	0000	0000	4a80	-6
56	7a01	0000	0000	0000	0
58	0000	7a01	0000	0000	0
60	0000	0000	7a01	0000	0
62	0000	0000	0000	7a01	-5
64	06c0	0000	0000	0000	0
66	xxxx	06c0	0000	0000	0
68	xxxx	xxxx	06c0	0000	0
70	xxxx	xxxx	xxxx	06c0	2
72	xxxx	xxxx	xxxx	xxxx	x
74	xxxx	xxxx	xxxx	xxxx	x

BEQ Without NOP's

[illegible]

BNE Test 1

PC	IFID_IR	IDEX_IR	EXMEM_IR	MEMWB_IR	WD
0	0000	xxxx	xxxx	xxxx	x
2	8100	0000	xxxx	xxxx	x
4	8202	8100	0000	xxxx	x
6	0000	8202	8100	0000	0
8	0000	0000	8202	8100	5
10	0000	0000	0000	8202	7
12	66c0	0000	0000	0000	0
14	0000	66c0	0000	0000	0
16	0000	0000	66c0	0000	0
18	0000	0000	0000	66c0	1
20	b305	0000	0000	0000	0
22	0000	b305	0000	0000	0
24	0000	0000	b305	0000	0
30	0000	0000	0000	b305	-1
32	0000	0000	0000	0000	0
34	0000	0000	0000	0000	0
36	0000	0000	0000	0000	0
38	8100	0000	0000	0000	0
40	8202	8100	0000	0000	0
42	0000	8202	8100	0000	0
44	0000	0000	8202	8100	5
46	0000	0000	0000	8202	7
48	4a80	0000	0000	0000	0
50	0000	4a80	0000	0000	0
52	0000	0000	4a80	0000	0
54	0000	0000	0000	4a80	-8
56	7a01	0000	0000	0000	0
58	0000	7a01	0000	0000	0
60	0000	0000	7a01	0000	0
62	0000	0000	0000	7a01	-7
64	06c0	0000	0000	0000	0
66	xxxx	06c0	0000	0000	0
68	xxxx	xxxx	06c0	0000	0
70	xxxx	xxxx	xxxx	06c0	-2
72	xxxx	xxxx	xxxx	xxxx	x
74	xxxx	xxxx	xxxx	xxxx	x

BNE Test 2

PC	IFID_IR	IDEX_IR	EXMEM_IR	MEMMB_IR	WD
0	0000	xxxx	xxxx	xxxx	x
2	8100	0000	xxxx	xxxx	x
4	8202	8100	0000	xxxx	x
6	0000	8202	8100	0000	0
8	0000	0000	8202	8100	7
10	0000	0000	0000	8202	5
12	66c0	0000	0000	0000	0
14	0000	66c0	0000	0000	0
16	0000	0000	66c0	0000	0
18	0000	0000	0000	66c0	0
20	b305	0000	0000	0000	0
22	0000	b305	0000	0000	0
24	0000	0000	b305	0000	0
26	0000	0000	0000	b305	0
28	9102	0000	0000	0000	0
30	9200	9102	0000	0000	0
32	0000	9200	9102	0000	0
34	0000	0000	9200	9102	2
36	0000	0000	0000	9200	0
38	8100	0000	0000	0000	0
40	8202	8100	0000	0000	0
42	0000	8202	8100	0000	0
44	0000	0000	8202	8100	5
46	0000	0000	0000	8202	7
48	4a80	0000	0000	0000	0
50	0000	4a80	0000	0000	0
52	0000	0000	4a80	0000	0
54	0000	0000	0000	4a80	-8
56	7a01	0000	0000	0000	0
58	0000	7a01	0000	0000	0
60	0000	0000	7a01	0000	0
62	0000	0000	0000	7a01	-7
64	06c0	0000	0000	0000	0
66	xxxx	06c0	0000	0000	0
68	xxxx	xxxx	06c0	0000	0
70	yyyy	yyyy	yyyy	06c0	-2

BNE Without NOP's

[illegible]